

## EE 460R - Lab 1 Report

Name : Haley Alexander (ha5722)

Verified by (TA) :

Date (TA) :

### Inverter Characterization:

1. Please fill this table from your simulation results: Truthful

<b>C(fF)</b>	<b>Slew(ps)</b>	<b>Tr(ps)</b>	<b>Tf(ps)</b>
100	10	10	7.02
100	30	9.9	10.26
100	50	33	9.33
300	10	16	3.9
300	30	29.8	21.99
300	50	7.02	22.15
500	10	7.01	7.02
500	30	7.02	6.71
500	50	9.33	10.96

Please fill this table from your simulation results: Theoretical


<b>C(fF)</b>	<b>Slew(ps)</b>	<b>Tr(ps)</b>	<b>Tf(ps)</b>
100	10	10	10.02
100	30	9.9	10.26
100	50	10.01	9.33
300	10	16	12.2
300	30	19.8	11.99
300	50	17.02	12.15
500	10	17.01	17.02
500	30	17.02	16.71

500	50	17.33	17.96
-----	----	-------	-------

2. Attach the following 4 graphs with this report:


Graph A1: plot  $T_r$  against  $C$  (keeping slew constant)

Used Slew of 10

 


Graph A2: plot  $T_f$  against  $C$  (keeping slew constant)

Used Slew of 10

 


Graph B1: plot  $T_r$  against slew (keeping  $C$  constant)

Used 100fF

 

 Graph B2: plot  $T_f$  against slew (keeping C constant)  
Used 300fF



### Memory Cell:


1. Area of the 4-bit cell
  - a. Length of the cell: 9.98  $\mu\text{m}$
  - b. Width of the cell: 16  $\mu\text{m}$
  - c. Final Area: 159.68 sq microns



2. Describe the techniques used for area minimization:
  - a. Minimize the length of wires for the inputs
  - b. Tried to combine transistors together
  - c. Used different metal layers to allow crossovers which minimize width
  - d. Sharing wells
  - e. Using HVH design protocol
3. Testing of the 4-bit cell:
  - a. DRC Pass (Yes/No):
  - b. LVS Pass (Yes/No):
  - c. Extract Report Clean (Yes/No):
  - d. Cell works for “writing 0011 - reading - writing 0101 - reading” (Yes/No):


If any answer above is “No”, please explain the issues faced:

Enclosures Required: (In this order)

 
1. The 4 graphs as required by “Inverter Characterization” for  $T_r$  and  $T_f$




  

 

 2. HSPICE waveform for ( $T_r$ ,  $T_f$ ) for the 'max load and max slew case



 

### 3. \*.sp file used in HSPICE to test the 4bit SRAM cell

\*\*\*\*\*

.global

\*\*\*\*\*change the slew\*\*\*\*\*

\*.param risefall = 10p

\*\*\*\*\*

\*\*\*\*\*change the cap\*\*\*\*\*

\*capout INV\_OUT 0 100f

\*\*\*\*\*

\*\*\*\*\*Pin Specification\*\*\*\*\*

\*\* Pin orders should be matched with 'inverter.pex.netlist' \*\*\*\*

x1 SC SA DC0 DC2 DC1 DC3 DB0 DB3 DB1 DB2 DA0 DA1 DA3 DA2 SB GND! VDD!

FourBitMem

\*\*\*\*\*

VGND GND! 0 0

VVDD VDD! 0 1

.TEMP 25

Vdc3 dc3 0 pwl (0n 0 0.05n 0 20n 0 20.05n 1 35n 1 35.05n 0 50n 0 70n 0)

Vdc2 dc2 0 pwl (0n 0 0.05n 0 20n 0 20.05n 0 35n 0 35.05n 1 50n 1 70n 1)

Vdc1 dc1 0 pwl (0n 1 0.05n 1 20n 1 20.05n 0 35n 0 35.05n 0 50n 0 70n 0)

Vdc0 dc0 0 pwl (0n 1 0.05n 1 20n 1 20.05n 0 35n 0 35.05n 1 50n 1 70n 1)

```
Vsc sc 0 pwl (0n 0 5n 0 5.05n 1 10n 1 10.05n 0 35n 0 35.05n 1 40n 1 40.05n 0 70n 0)
Vsa sa 0 pwl (0n 0 15n 0 15.05n 1 20n 1 20.05n 0 45n 0 45.05n 1 50n 1 50.05n 0 70n 0)
Vsb sb 0 pwl (0n 0 25n 0 25.05n 1 30n 1 30.05n 0 55n 0 55.05n 1 60n 1 60.05n 0 70n 0)
```

\*\*\*\*\* Adjust stop time for the simulation to get the waveform you want \*\*\*\*\*

```
.tran 10p 90n
```


\*\*\*\*\*

```
.op
```

```
.option post
```


```
.END
```
 
#### 4. HSPICE waveform for 4bit SRAM cell


 
#### 5. Layout with rulers showing the width and length of the 4bit cell





Prepare to demo/show:

1. 1-bit SRAM schematic and Layout
2. 4-bit SRAM schematic and Layout
3. DRC/LVS/Extraction Report for the 4bit SRAM cell